



Is Now Part of



**ON Semiconductor®**

To learn more about ON Semiconductor, please visit our website at  
[www.onsemi.com](http://www.onsemi.com)

ON Semiconductor and the ON Semiconductor logo are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.



# AN-9113

## Bootstrap Circuit Design Guide for Motion SPM<sup>®</sup> Products

### Table of Contents

1.	Introduction of Bootstrap Circuit .....	2
1.1.	Bootstrap Circuit Operation .....	2
1.2.	Initial Charging .....	3
1.3.	Normal Operation .....	6
1.4.	C <sub>boot</sub> Selection Guide .....	8
1.5.	R <sub>boot</sub> Selection Guide .....	9
1.5.1.	Resistance Value of R <sub>boot</sub> .....	9
1.5.2.	Power Rating of R <sub>boot</sub> .....	9
1.6.	Dboot Selection Guide .....	10
1.7.	Integrated Bootstrap Circuit Information in Motion SPM <sup>®</sup> Products .....	10
1.8.	Required Precautions to Prevent Malfunction or Damage .....	10
1.9.	Frequently Asked Questions and Answers .....	11
2.	Related Resources .....	12

# 1. Introduction of Bootstrap Circuit

To drive high side power switches in three phase inverters, three additional isolated and floated control supplies are required because floating control supply is necessary to drive each high side. These additional three floating control supplies can be replaced by a bootstrap circuit which is simple and inexpensive. A bootstrap circuit consists of three components; bootstrap diode ( $D_{boot}$ ), bootstrap capacitor ( $C_{boot}$ ) and bootstrap resistor ( $R_{boot}$ ). In bootstrap circuit design, many considerations are required to select proper bootstrap components based on electrical characteristics of the device, including Motion SPM<sup>®</sup> products and user's operating conditions.

## 1.1. Bootstrap Circuit Operation

The charged voltage of  $C_{boot}$  ( $V_{BS}$ ) operates as a floating supply to control a high side power switch. It is necessary to charge  $C_{boot}$  initially because  $V_{BS}$  is 0 V at initial state.  $V_{BS}$  should be higher than its under-voltage reset level (generally more than 13 V is recommended) to operate high side power switches according to high side PWM input.  $C_{boot}$  is charged from a low side 15 V control supply ( $V_{DD}$ ) when the low side power switch or diode is turned on. Figure 1 shows  $C_{boot}$  charging path when low side IGBT is turned on. In initial charging stage, all three  $C_{boot}$  can be charged by one phase IGBT turning on when output is connected to the motor load, but charging time might be longer than all three phase turn on due to series resistance and inductance of load. Recommendations and a guide of initial charging are explained in section 1.2. Figure 2 shows a  $C_{boot}$  charging path when a low side diode is turned on during inverter operation.

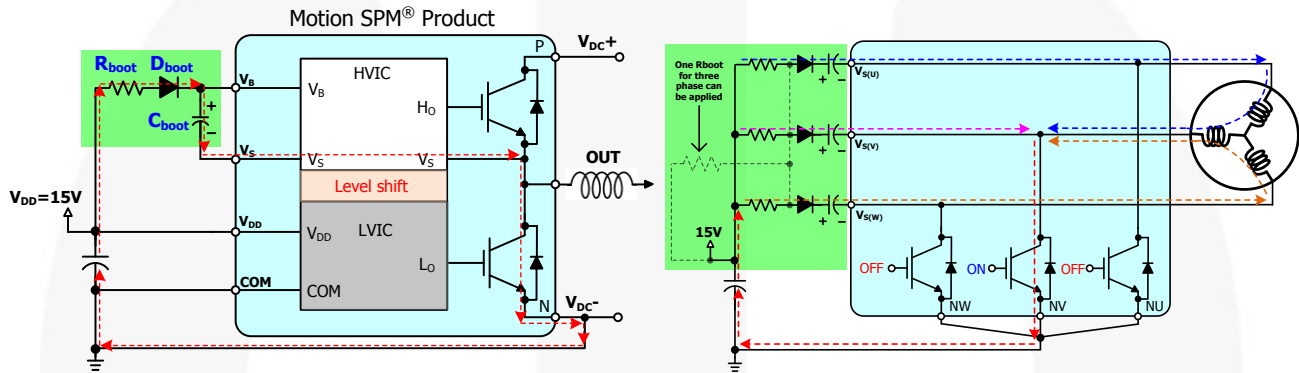


Figure 1. Charging Mechanism of  $C_{boot}$  by Low Side Power Switch Turn On

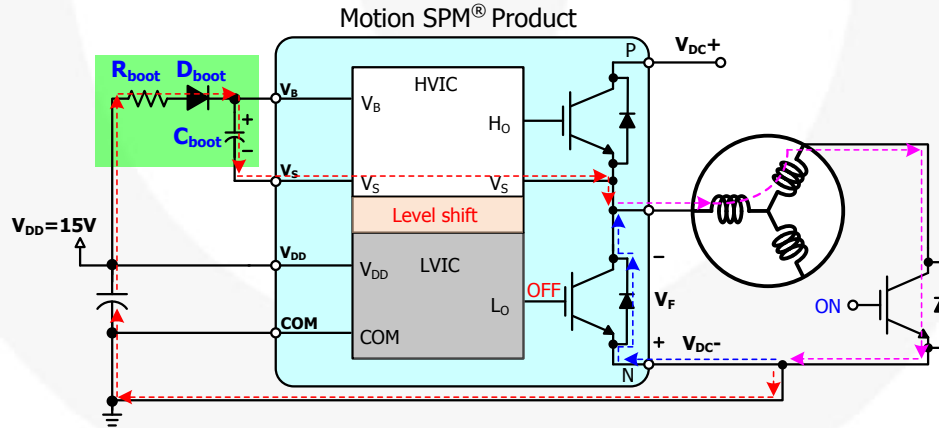


Figure 2. Charging Mechanism of  $C_{boot}$  by Low Side Diode Freewheeling

$V_{BS}$  can be charged up to below value according to operation state.

- A. Initial charging and low side power switch turning on. ( $I_{QBS}$ : Quiescent current of  $V_{BS}$  supply)

$$V_{BS} = V_{DD} - (I_{QBS} \times R_{boot}) - V_F \text{ of } D_{boot} \text{ at } I_{QBS} - V_{cesat} \text{ or } V_{dson} \text{ of low side switch at } I_{QBS}$$

- B. Low side Diode freewheeling.

$$V_{BS} = V_{DD} - (I_{QBS} \times R_{boot}) - V_F \text{ of } D_{boot} \text{ at } I_{QBS} + V_F \text{ of low side Diode at operating current}$$

A  $C_{boot}$  is discharged by current consumed for high side driving. The current consumed is consistent with quiescent current of high side gate driver ( $I_{QBS}$ ), level shift driving and gate charge of power switch ( $Q_g$ ).

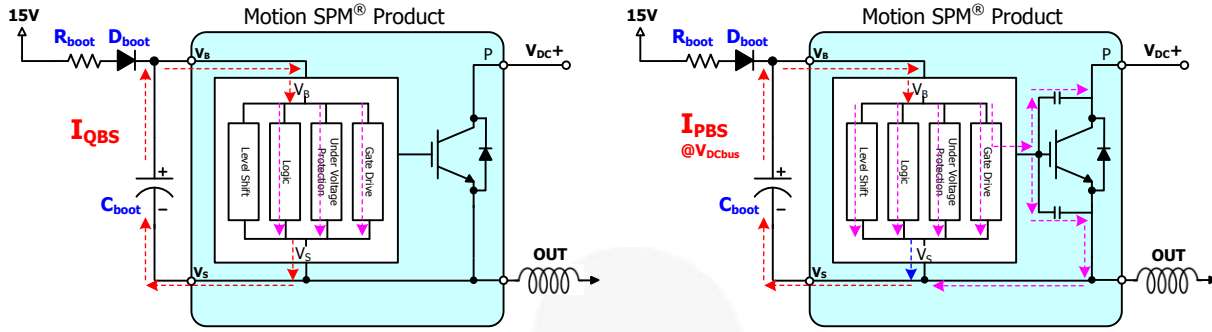


Figure 3. Discharging Mechanism of  $C_{boot}$  (Left: Steady State, Right: High Side Power Switch Operate)

## 1.2. Initial Charging

First,  $C_{boot}$  should be charged up to proper  $V_{BS}$  for stable operation of high side. There are several methods for initial charging of  $C_{boot}$ . A suitable method needs to be applied based on system requirements. Points to be considered as system requirement are below.

- Capacitance of  $C_{boot}$  and resistance of  $R_{boot}$ .
- Over-current protection level from external shunt resistor.
- Target maximum initial charging time.

$C_{boot}$  is initially charged from 0 V by low side turn on. Required charging time ( $t_{charge}$ ) depends on duty ratio of the low side PWM input, capacitance of  $C_{boot}$  and resistance of  $R_{boot}$ .  $C_{boot}$  charging with full duty ( $D=1$ , Full on) is preferred to reduce initial charging time, however sometimes  $C_{boot}$  charging with specific duty is required considering the limitation of  $R_{boot}$  pulse power rating or control supply current capability and so on. Examples of a timing chart and required charging time for  $V_{BS}$  supply are shown in Figure 4. Initial charging time graph is based on three  $R_{boot}$  for three phase condition. If one  $R_{boot}$  is used for all three phases, three times longer  $t_{charge}$  is required compared with three  $R_{boot}$  condition. It is noted that  $C_{boot}$  should be charged up to under-voltage  $V_{BS}$  reset level (UVBSR) when it is charged initially for high side operation.

Recommended initial charging time is determined by equation (1).

$$\begin{aligned} \text{MOSFET version: Initial charging time} &= -R_{boot} \times C_{boot} \times \frac{\ln\left(1 - \frac{UVBSR \text{ max.}}{VDD - D_{boot} V_{th} @ IQBS \text{ max.}}\right)}{\text{low side on duty}} \\ \text{IGBT version: Initial charging time} &= -R_{boot} \times C_{boot} \times \frac{\ln\left(1 - \frac{UVBSR \text{ max.}}{VDD - D_{boot} V_{th} @ IQBS \text{ max.} - IGBT \text{ CE } V_{th} @ IQBS \text{ max.}}\right)}{\text{low side on duty}} \end{aligned} \quad (1)$$

Where;

$IQBS \text{ max.}$  is maximum quiescent current of  $V_{BS}$  supply.

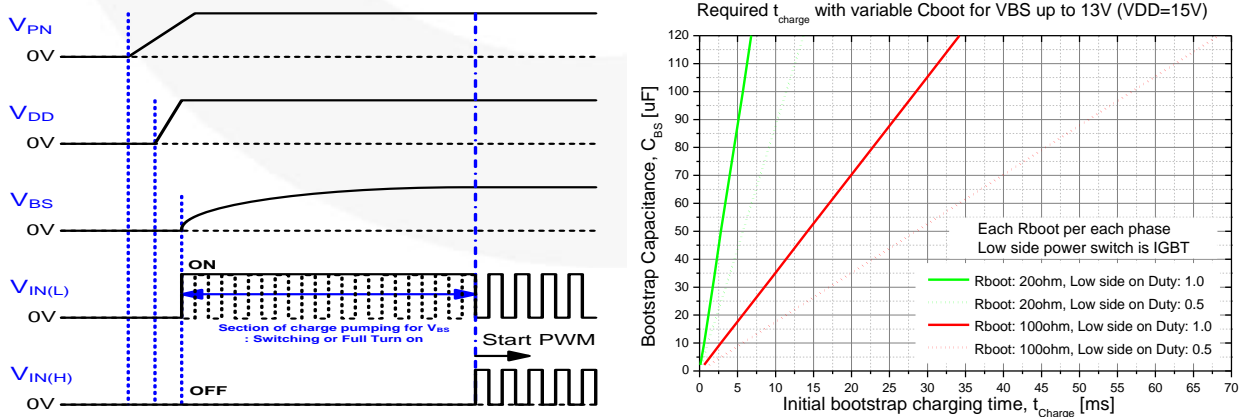


Figure 4. Timing Chart and Required Charging Time for Initial Charging of  $C_{boot}$

Examples of initial  $C_{boot}$  charging waveform are shown in Figure 5 under full turn on and switching pulses conditions. Hardware design engineers need to select proper values of  $R_{boot}$  and initial charging duty ratio based on target maximum  $V_{BS}$  charging time. High side PWM input should be operated after  $V_{BS}$  supply is sufficiently charged. For a stable operation, it is recommended to operate high side power switch after  $V_{BS}$  supply is charged more than 13 V.

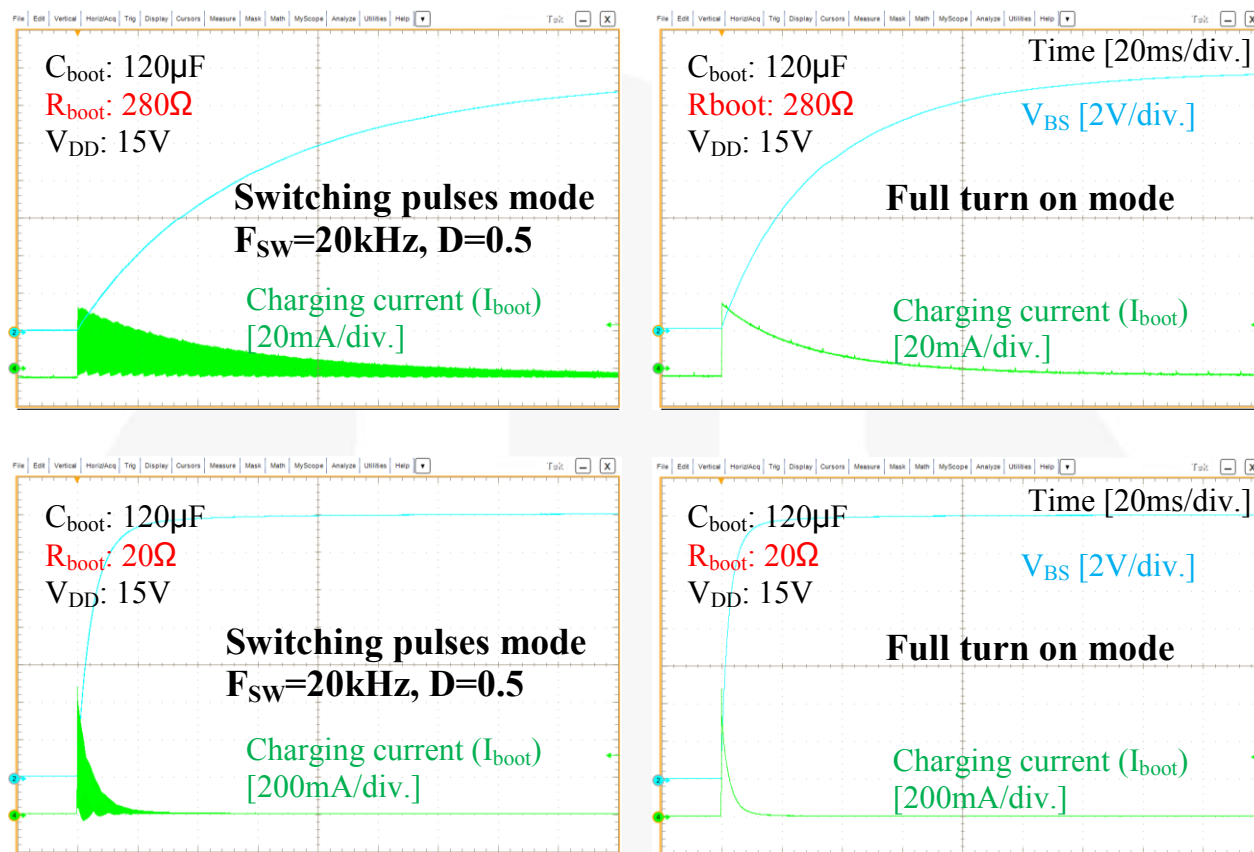


Figure 5. VBS supply initial charging waveforms with variable  $R_{boot}$  and Duty ratio

There is an Under-Voltage Lockout function (UVLO) in gate driver to prevent power switches from operating under a low gate voltage condition which may cause large power loss of power switches. This UVLO protection function can be triggered when  $V_{BS}$  supply is initially charged with low  $R_{boot}$ , large  $C_{boot}$  and high duty ratio as shown in Figure 6. To prevent this unexpected fault event, switching pulses with low duty or enough source capacitance for 15 V control supply are recommended.

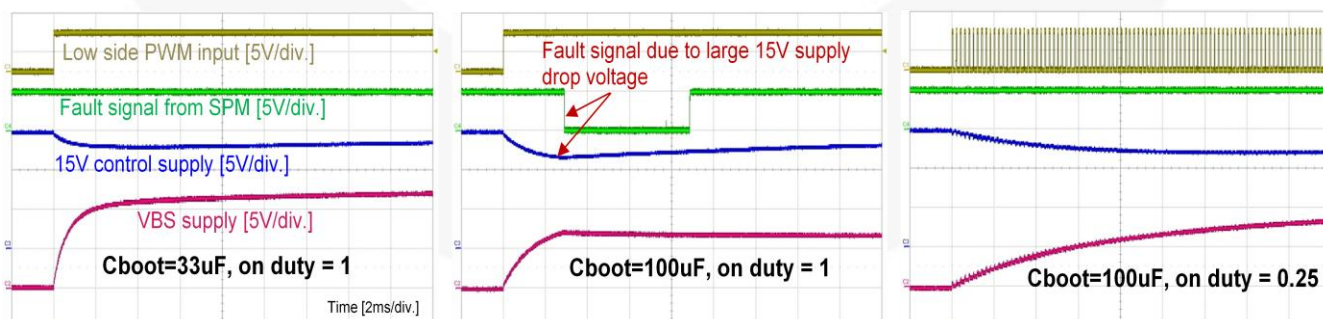


Figure 6. Initial Charging According to Bootstrap Capacitance and Charging Method  
(Ref. Condition:  $V_{DD} = 15\text{ V} / 300\text{ mA}$ ,  $V_{DD}$  Capacitor =  $220\text{ }\mu\text{F}$ ,  $C_{boot} = 100\text{ }\mu\text{F}$ ,  $R_{boot} = 20\text{ }\Omega$ )

Generally, a low power inverter uses a MOSFET as a power switch. Thus, Over-Current Protection (OCP) level is low because the applied MOSFET's current rating is low. If three shunt resistors are connected to each low side N terminal, all three low side turn on is recommended for  $C_{boot}$  initial charging to prevent potential risk of OCP since one low side turn on causes increase of current at one shunt resistor. Therefore, all three MOSFET turn on is recommended when  $C_{boot}$  is charged initially if three shunt is used for current sensing considering OCP level. For 15 V supply point of view, one low side turn on can be recommended because peak bootstrap current ( $I_{boot\_peak}$ ) is lower than that of all three low side turn on due to series resistance and inductance in load. On the contrary to this, voltage drop in shunt R is reduced by one low side turn on in one shunt R system due to a small  $I_{boot}$ .

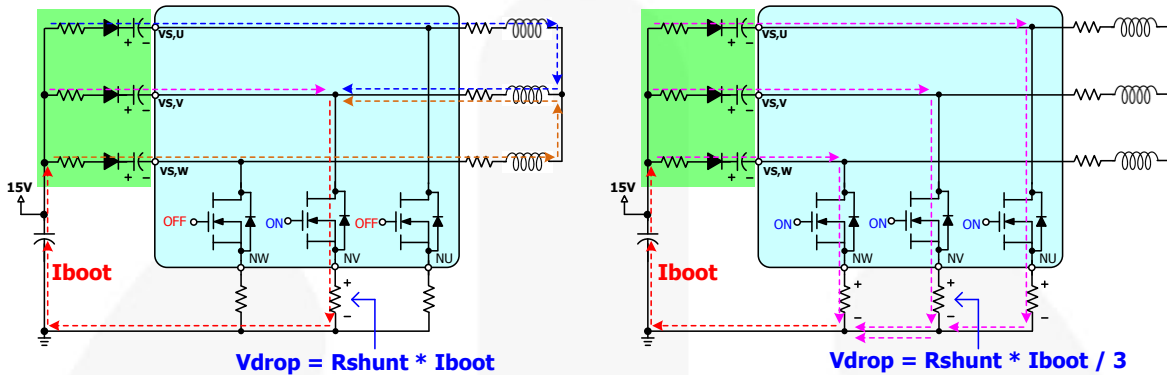


Figure 7. Initial Charging Mechanism according to Low Side Turn On State in Three Shunt R ( $I_{boot}$  peak value of left schematic is lower than that of right schematic due to the impedance of load)

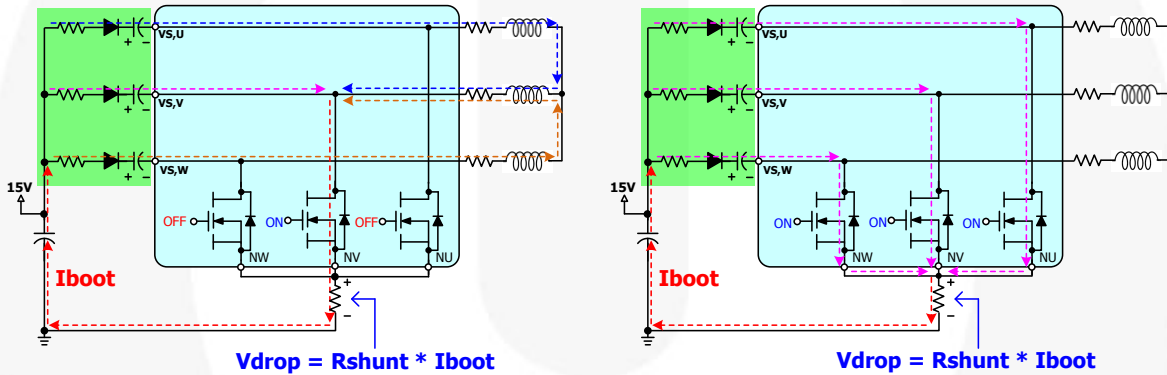


Figure 8. Initial Charging Mechanism according to Low Side Turn On State in One Shunt R

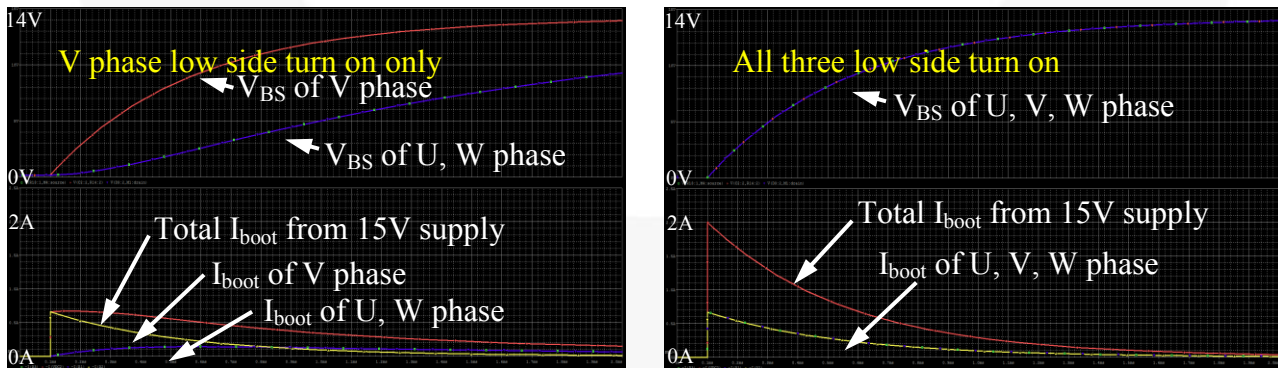


Figure 9. Initial charging of each phase according to low side turn on state (Each  $R_{boot} = 20 \Omega$ , Each  $C_{boot} = 22 \mu F$ , Load impedance =  $20 \Omega + 5 mH$ )

For initial  $C_{boot}$  charging by bootstrap circuit, it is recommended to consider:

- To reduce risk of UVLO fault: switching with duty ratio and increase of 15 V supply capacitance (or decrease of  $C_{boot}$ ) needs to be considered.
- To reduce risk of OCP fault: three shunt R condition  $\rightarrow$  three low side turn on, one shunt R condition  $\rightarrow$  one low side turn on.
- To reduce total  $I_{boot}$  from 15 V supply due to lack of output current: one low side switching with small duty is recommended.



### 1.3. Normal Operation

$V_{BS}$  supply voltage ripple and average values are influenced by  $R_{boot}$ ,  $C_{boot}$  and operating conditions. For stable operation, this ripple voltage should be kept within a recommended  $V_{BS}$  supply voltage range. In inverter operation,  $C_{boot}$  is charged when low side IGBT (MOSFET) or diode are conducted. When high side power switch operates, low average  $V_{BS}$  voltage causes increase of switching loss and conduction loss due to lower gate control voltage. And also high side gate driver's under-voltage lockout for  $V_{BS}$  supply should be considered.  $V_{BS}$  supply voltage should be higher than UVLO reset level before high side power switches operate if minimum  $V_{BS}$  supply voltage is lower than UVLO detection level.

Figure 10 shows explanation and recommendations of  $V_{BS}$  supply voltage during inverter operations based on Motion SPM® products with variable  $R_{boot}$  and  $C_{boot}$  values.

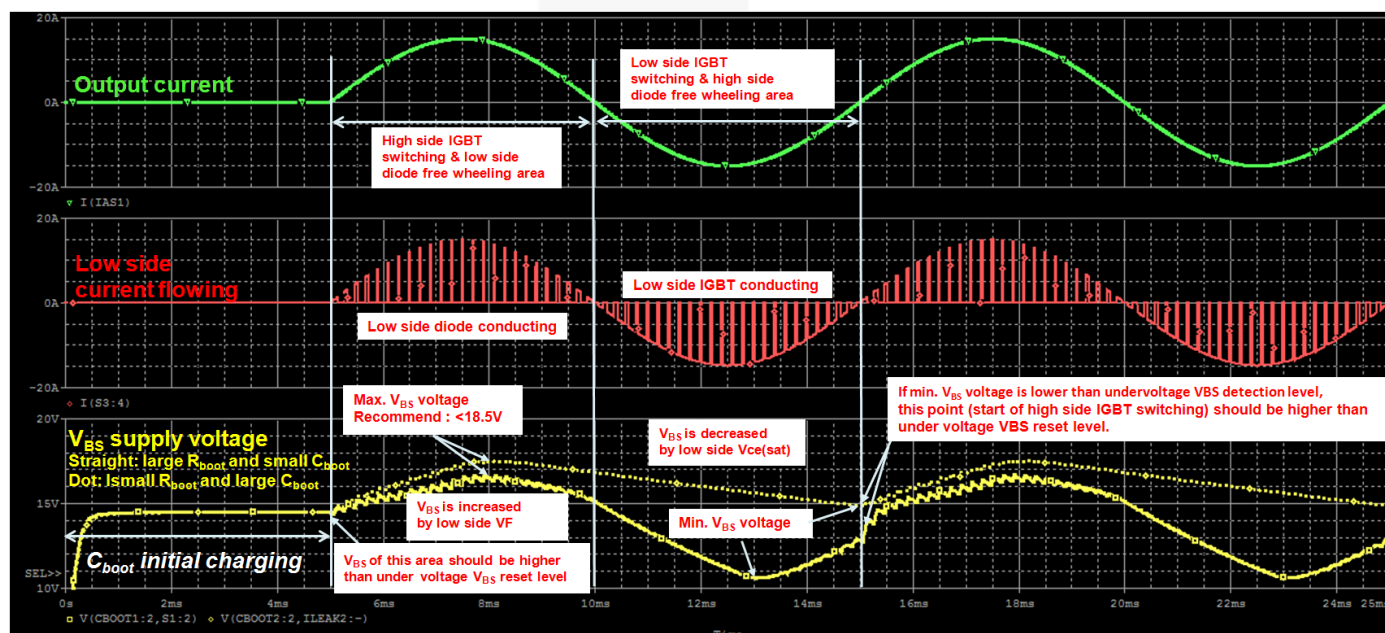


Figure 10. Example Waveform of  $I_{OUT}$  vs.  $V_{BS}$  supply voltage

$V_{BS}$  supply ripple voltage and average voltage are influenced mainly by factors below. Please note that below results came from a general trend and can be different depending on device characteristics and conditions.

- A. Small  $C_{boot}$  → Ripple voltage of  $V_{BS}$  supply increases.
- B. Large  $R_{boot}$  during → Average voltage of  $V_{BS}$  supply decreases.
- C. Large Shunt R (in three shunt resistors for each N terminal) → Average voltage of  $V_{BS}$  supply decreases.
- D. High  $V_{BS}$  supply current consumption → Average voltage of  $V_{BS}$  supply decreases.
- E. High operating current → Average voltage of  $V_{BS}$  supply increases, ripple voltage of  $V_{BS}$  supply increases.
- F. Low output current frequency →  $V_{BS}$  supply ripple increases.
- G. High modulation index (M.I) → Average voltage of  $V_{BS}$  supply decreases.
- H. High switching frequency → Average voltage of  $V_{BS}$  supply decreases.

Figure 11 shows comparison results of  $V_{BS}$  supply voltage by variable condition.

Below condition is applied as a reference condition for each comparison.

- A. Ideal circuit without any stray impedance in the loop.
- B.  $C_{boot}$  initial charging mode: Low side IGBT full on for 15 ms.
- C. 15A rated IGBT/diode Motion SPM® product, three shunt R at each N-terminal, High side IGBT  $Q_g = 45$  nC
- D.  $R_{boot} = 20 \Omega$ ,  $C_{boot} = 22 \mu F$ , Shunt R at N-terminal = 25 m $\Omega$ ,  $V_{BS}$  supply current consume = 100  $\mu A$
- E.  $V_{DC} = 300$  V,  $V_{DD} = 15$  V,  $f_{SW} = 10$  kHz,  $F_O = 100$  Hz,  $I_{OUT} = 15$  A<sub>pk</sub>, M.I = 0.9, SVPWM

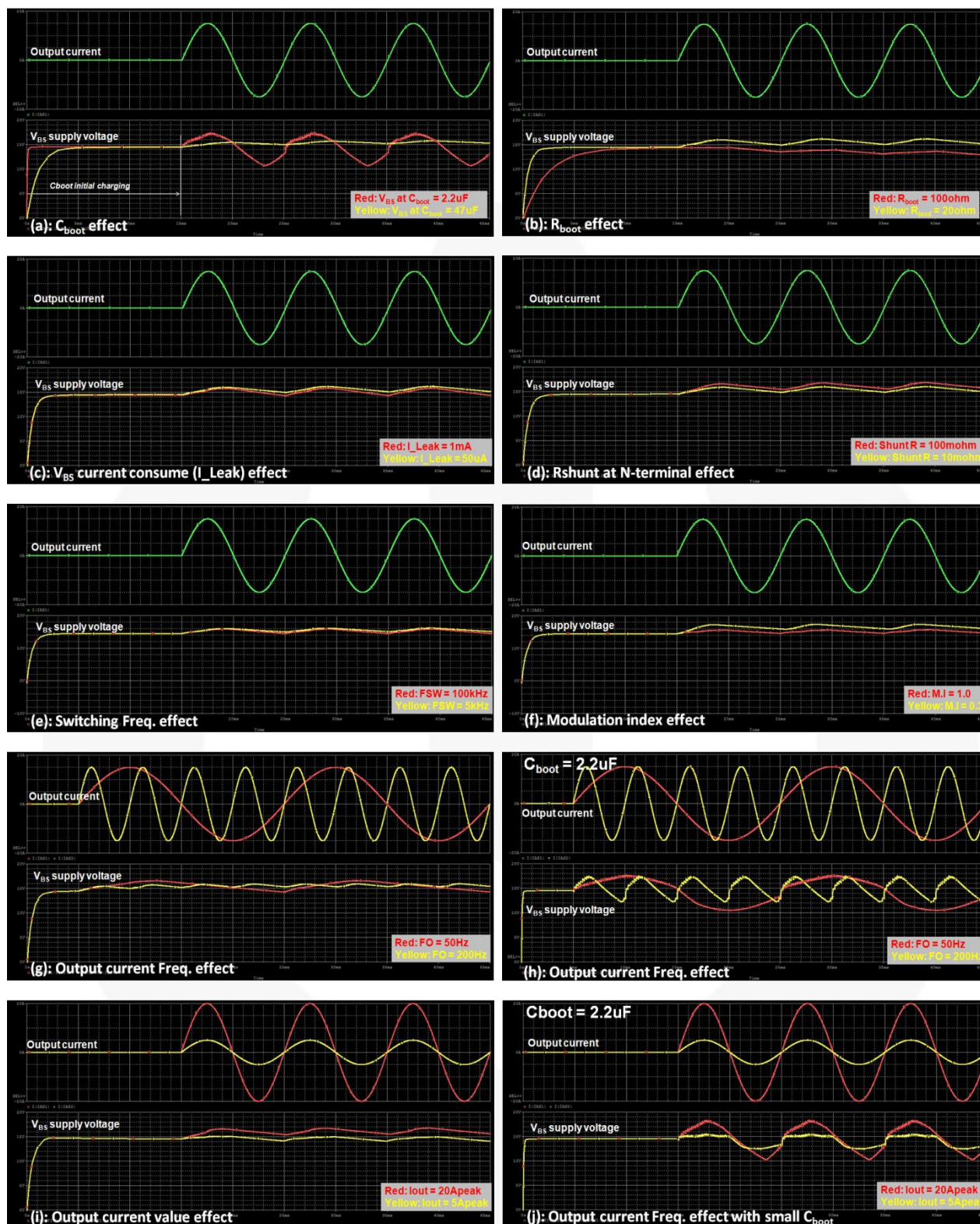


Figure 11. Example waveform of  $I_{OUT}$  vs.  $V_{BS}$  supply voltage according to parameters of passive components and operating condition



## 1.4. C<sub>boot</sub> Selection Guide

The bootstrap capacitance needs to be selected based on V<sub>BS</sub> supply positive and negative ripple voltage considering PWM methods. In trapezoidal PWM, sufficiently large C<sub>boot</sub> is recommended because V<sub>BS</sub> supply can go very low due to long discharge time without charging time. Allowable discharge voltage of C<sub>boot</sub> (ΔV<sub>BS</sub>) is determined by Under-voltage V<sub>BS</sub> Detection (UVBSD) level. Usually, max. UVBSD is around 12.5 V in most of motion SPM<sup>®</sup> products. Thus, recommended allowable ΔV<sub>BS</sub> is 2~3 V.

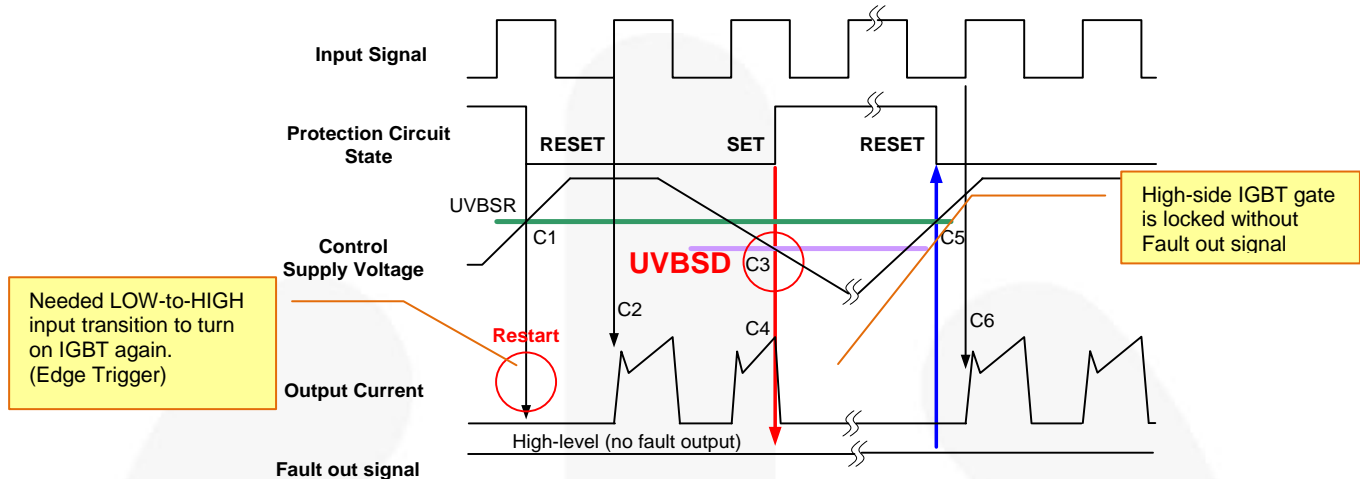


Figure 12. Timing Chart of High-Side Under-Voltage Protection Function

Discharge voltage of C<sub>boot</sub> (ΔV<sub>BS</sub>) is calculated by equation (2).

$$\Delta V_{BS} = \frac{\Delta t \times I_{Leak}}{C_{boot}} \quad (2)$$

Δt: maximum time of C<sub>boot</sub> discharging (All PWM 0V or high side turn on period);

ΔV<sub>BS</sub>: the allowable discharge voltage of the C<sub>boot</sub> and

I<sub>Leak</sub>: maximum discharge current of the C<sub>boot</sub>. Mainly via the following mechanisms:

- Quiescent current to the high-side control circuit in HVIC (IQBS).
- C<sub>boot</sub> leakage current (ignored for non-electrolytic capacitors).

In sine-wave PWM with dead time, V<sub>BS</sub> supply ripple voltage is varied by many factors. This ripple voltage is reduced efficiently by increase of C<sub>boot</sub> capacitance. However, many users want to use small C<sub>boot</sub> in low power system for cost reduction. It is necessary to measure V<sub>BS</sub> voltage under the overload condition to check whether V<sub>BS</sub> is within recommended range. Figure 13 shows a selection guide to determine proper C<sub>boot</sub> value in the system.

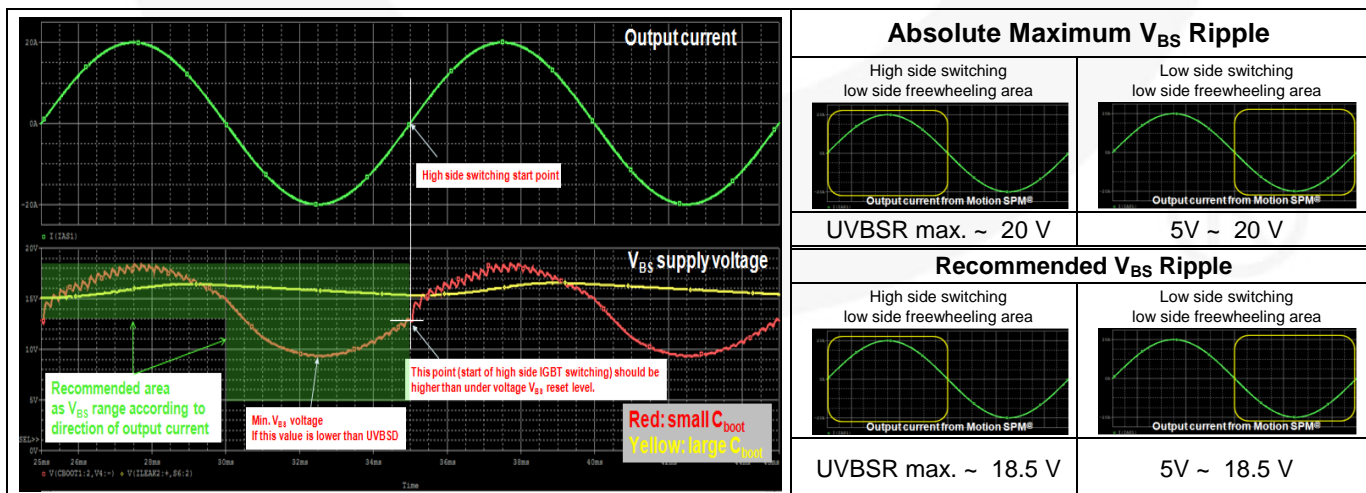


Figure 13. V<sub>BS</sub> Supply Ripple Voltage Waveform, Maximum and Recommended Values

## 1.5. R<sub>boot</sub> Selection Guide

### 1.5.1. Resistance Value of R<sub>boot</sub>

Both initial charging time from 0 V to UVBSR as explained in page 3 of section ‘Initial Charging’ and allowable peak current should be considered in selecting the resistance value

Required initial charging time defined by equations below:

$$\text{MOSFET version: Initial charging time} = -R_{boot} \times C_{boot} \times \frac{\ln\left(1 - \frac{UVBSR \text{ max.}}{VDD - D_{boot} V_{th} @ IQBS \text{ max.}}\right)}{\text{low side on duty}} \quad (3)$$

$$\text{IGBT version: Initial charging time} = -R_{boot} \times C_{boot} \times \frac{\ln\left(1 - \frac{UVBSR \text{ max.}}{VDD - D_{boot} V_{th} @ IQBS \text{ max.} - IGBT \text{ CE } V_{th} @ IQBS \text{ max.}}\right)}{\text{low side on duty}} \quad (4)$$

Required min. R<sub>bs</sub> considering peak inrush current:

$$\text{MOSFET version: Peak inrushed current} = \frac{(VDD - D_{boot} V_{th} - IGBT \text{ CE } V_{th} @ IQBS \text{ max.})}{R_{boot}} \quad (5)$$

$$\text{IGBT version: Peak inrushed current} = \frac{(VDD - D_{boot} V_{th} @ IQBS \text{ max.} - IGBT \text{ CE } V_{th} @ IQBS \text{ max.})}{R_{boot}} \quad (6)$$

Generally, each 0.6 V for both D<sub>boot</sub> V<sub>th</sub> and IGBT CE V<sub>th</sub> can be available as its voltage drop.

A resistor R<sub>boot</sub> must be added in series with the bootstrap diode to slow down the d<sub>VBS</sub>/d<sub>t</sub>. It also determines the time to charge the bootstrap capacitor during system operation after initial charging. The bootstrap capacitor has to be charged by ΔV during the minimum ON pulse width of low-side MOSFET or the minimum OFF pulse width of high-side MOSFET, t<sub>o</sub>. Therefore, the value of R<sub>boot</sub> needs to be determined by equation (7).

$$R_{boot} = \frac{(VDD - VBS) \times t_o}{C_{boot} \times \Delta VBS} \quad (7)$$

### 1.5.2. Power Rating of R<sub>boot</sub>

In terms of power rating of R<sub>boot</sub>, pulse power rating should be considered for initial charging of bootstrap capacitor. To use a large bootstrap capacitor, high pulse power rating is required for the bootstrap resistor. An example of resistor pulse power rating is shown in Figure 14.

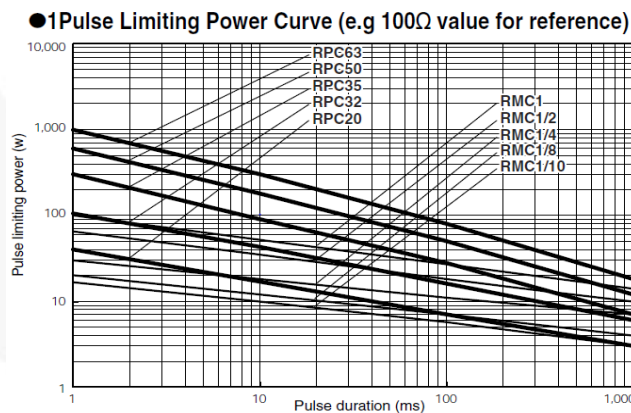


Figure 14. Example of Pulse Power Curve of Resistor (from KAMAYA OHM)

Required power and pulse duration times are calculated by equation (8) when C<sub>boot</sub> is initially charged.

$$\text{MOSFET version pulse power} = \frac{(VDD - D_{boot} V_{th} @ IQBS \text{ max.})^2}{R_{boot}}$$

$$\text{IGBT version pulse power} = \frac{(VDD - D_{boot} V_{th} @ IQBS \text{ max.} - IGBT \text{ CE } V_{th} @ IQBS \text{ max.})^2}{R_{boot}} \quad (8)$$

$$\text{Pulse duration time} = 0.5 \times R_{boot} \times C_{boot}$$

## 1.6. Dboot Selection Guide

When high side IGBT (MOSFET) or diode conducts, the bootstrap diode (DBS) supports the entire bus voltage. Hence the withstand voltage higher than rated voltage of Motion SPM<sup>®</sup> product is recommended. It is important that this diode should be a fast recovery (recovery time < 100 ns) device to minimize the amount of charge that is fed back from the bootstrap capacitor into the  $V_{DD}$  supply. Similarly, the high voltage reverse leakage current is important if the capacitor has to store charge for long periods of time.

## 1.7. Integrated Bootstrap Circuit Information in Motion SPM<sup>®</sup> Products


Many Motion SPM<sup>®</sup> product provides integrated bootstrap circuit for user's convenience.

**Table 1. Integrated Bootstrap Circuit information and Allowable max.  $C_{boot}$  values**

Series of Motion SPM <sup>®</sup> products	Related Part Name	Max. Repetitive Reverse Voltage	Integrated Bootstrap Circuit	Allowable Max. $C_{boot}$
Motion SPM 5, V2	FSB50xx0Ax FSB50xx0SFx	600 V	Bare bootstrap diode $R_{boot}$ is around 20 $\Omega$	Up to 220 $\mu$ F
Motion SPM 8	FNB8xx60Tx	600 V	Integrated in driver $R_{boot}$ is around 280 $\Omega$	Up to 220 $\mu$ F
Motion SPM 55, V2	FNx5xx60TDx	600 V	Integrated in driver $R_{boot}$ is around 280 $\Omega$	Up to 220 $\mu$ F
Motion SPM 45H	FNx4xx60xx	600 V	Bare bootstrap diode $R_{boot}$ is around 20 $\Omega$	Up to 220 $\mu$ F
Motion SPM 3, V4~V6	FSBBxxCH60x FNB3xx60T	600 V	Bare bootstrap diode $R_{boot}$ is around 20 $\Omega$	Up to 220 $\mu$ F
Motion SPM 2	FNx2xx60	600 V	Bare bootstrap diode No $R_{boot}$ (external $R_{boot}$ is required)	Limited by external $R_{boot}$
	FNx2xx12Ax	1200 V		

## 1.8. Required Precautions to Prevent Malfunction or Damage

For output current sensing,  $V_{BS}$  supply can be used for current sensor circuit. At this condition,  $V_{BS}$  supply current consumption is increased by additional current consumption for current sensor circuit. This should be considered for  $R_{boot}$  values because avg.  $V_{BS}$  voltage drop is large if  $R_{boot}$  value is high in this condition. Thus, high side shut down by UVBS or high power loss of high side by low control voltage can occur if large  $R_{boot}$  is used when  $V_{BS}$  supply current consumption is very high.

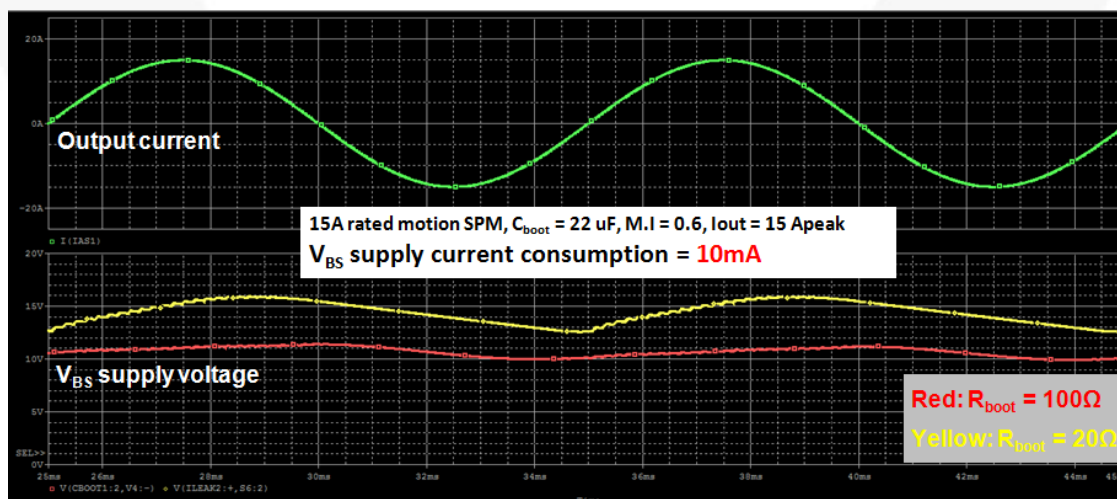

**Figure 15. Example waveform of  $I_{OUT}$  vs.  $V_{BS}$  supply voltage under the variable  $R_{boot}$  and high  $V_{BS}$  supply current consumption condition**

Small  $R_{boot}$  and  $C_{boot}$  can cause overcharging of  $C_{boot}$  when high side is turned by stray inductance and turn off  $di/dt$ . The  $C_{boot}$  can become overcharged, and the high side gate driver has damage by over-voltage stress if it exceeds the absolute maximum rating of high side gate driver. To prevent this situation proper selections of  $C_{boot}$  and  $R_{boot}$  are required considering overload condition like high operating current.

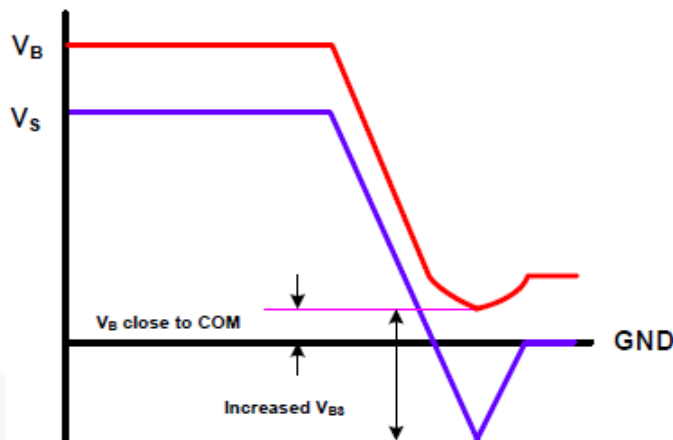


Figure 16. Typical Response of  $V_B$  and  $V_S$  when High Side Turn Off

## 1.9. Frequently Asked Questions and Answers

- A. Is it possible to use one  $R_{boot}$  for all three phase?  
 :Yes, one  $R_{boot}$  can be used as a common  $R_{boot}$ . Charging time can increase to charge parallel  $C_{boot}$ . Please refer to Section 1.1.
- B. There are over-current detection problem when  $C_{boot}$  is charged initially. How to prevent this event?  
 :Soft ware debugging to ignore OCP at initial charging  
 :In one shunt R configuration → One low side turn on to reduce total  $I_{boot}$  for all three  $C_{boot}$  initial charging  
 :Connect resistor between output (U, V, W) and GND (N-terminals or COM) for  $C_{boot}$  charging in advance before initial charging sequence (recommended resistor value is around several hundred of  $k\Omega$ )
- C. What is allowable maximum  $C_{boot}$ ?  
 :It depends on pulse power rating and resistance of  $R_{boot}$ .  
 :In Motion SPM® products which provides integrated bootstrap circuit, allowable max.  $C_{boot}$  is 220  $\mu F$ .
- D. Ceramic type capacitors can be used as  $C_{boot}$ ?  
 :Yes, ceramic capacitors can be used. Please select proper capacitance
- E. 7 times larger 15 V source capacitor is recommended to prevent UVLO fault. We want to apply large capacitance as  $C_{boot}$ . How can we reduce 15 V source capacitor without UVLO risk?  
 : Please refer to below recommended circuit.

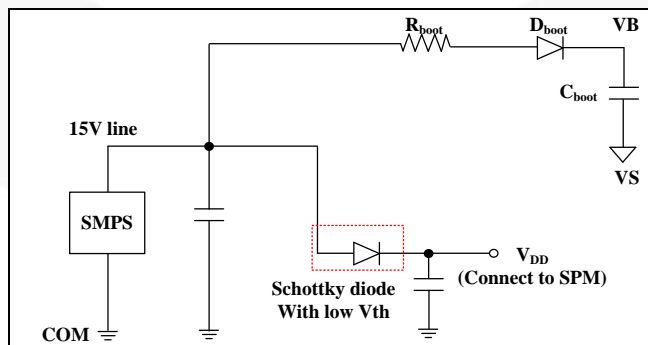


Figure 17. Recommended Circuit to Apply Small Source Capacitor



## 2. Related Resources

[AN-9096, Smart Power Module, Motion SPM® 55 Series User's Guide](#)

[AN-6067, Design and Application Guide of Bootstrap Circuit for High-Voltage Gate-Drive IC](#)

---

### DISCLAIMER

FAIRCHILD SEMICONDUCTOR RESERVES THE RIGHT TO MAKE CHANGES WITHOUT FURTHER NOTICE TO ANY PRODUCTS HEREIN TO IMPROVE RELIABILITY, FUNCTION, OR DESIGN. FAIRCHILD DOES NOT ASSUME ANY LIABILITY ARISING OUT OF THE APPLICATION OR USE OF ANY PRODUCT OR CIRCUIT DESCRIBED HEREIN; NEITHER DOES IT CONVEY ANY LICENSE UNDER ITS PATENT RIGHTS, NOR THE RIGHTS OF OTHERS.

### LIFE SUPPORT POLICY

FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF FAIRCHILD SEMICONDUCTOR CORPORATION.

As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, or (c) whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in significant injury to the user.

A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

## PUBLICATION ORDERING INFORMATION

### LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor  
19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA  
**Phone:** 303-675-2175 or 800-344-3860 Toll Free USA/Canada  
**Fax:** 303-675-2176 or 800-344-3867 Toll Free USA/Canada  
**Email:** [orderlit@onsemi.com](mailto:orderlit@onsemi.com)

**N. American Technical Support:** 800-282-9855 Toll Free  
USA/Canada

**Europe, Middle East and Africa Technical Support:**  
Phone: 421 33 790 2910

**Japan Customer Focus Center**  
Phone: 81-3-5817-1050

**ON Semiconductor Website:** [www.onsemi.com](http://www.onsemi.com)

**Order Literature:** <http://www.onsemi.com/orderlit>

For additional information, please contact your local  
Sales Representative